

# VLSI HW2

---

Name: 徐竣霆

Student ID: 110060012

## Some important design rule for .18

---

- $W_{cont} = 0.23$
- $S_{cont-diff} = 0.12$
- $W_{cont-diff} = 0.47$
- $S_{imp-diff} = 0.2$
- $S_{poly-cont} = 0.14$
- $S_{m1-m1} = 0.24$
- $S_{cont-cont} = 0.25$
- $S_{m2-m2} = 0.27$
- $W_{m1} = 0.23$
- $W_{m2} = 0.25$
- $W_{via(m1,m2)} = 0.25$
- $S_{diff-cont-poly} = 0.49$
- $S_{poly-cont-poly} = 0.51$
- $S_{poly-poly} = 0.25$
- $S_{poly-diff} = 0.2$
- $S_{m1-cont} = 0.1$





## The circuit diagram of my design and explaining my design

---

### HW2

### Graph

  

**Code**



```

**Your code**
.subckt INV in inv_out VDD GND
Mp1 inv_out in VDD VDD p_18 l=0.18u w=0.47u
Mn1 inv_out in GND GND n_18 l=0.18u w=0.47u
.ends

**Your design**
.subckt hw2_XOR A B C S VDD GND
**Your code**
Xinv1 A inv_A VDD GND INV
Xinv2 B inv_B VDD GND INV
Xinv3 C inv_C VDD GND INV
Mp1 n1 A VDD VDD p_18 l=0.18u w=0.47u
Mp2 n2 inv_A VDD VDD p_18 l=0.18u w=0.47u
Mp3 n3 B n1 VDD p_18 l=0.18u w=0.47u
Mp4 n3 inv_B n2 VDD p_18 l=0.18u w=0.47u
Mp5 n4 inv_B n1 VDD p_18 l=0.18u w=0.47u
Mp6 n4 B n2 VDD p_18 l=0.18u w=0.47u
Mp7 S inv_C n3 VDD p_18 l=0.18u w=0.47u
Mp8 S C n4 VDD p_18 l=0.18u w=0.47u
Mn1 n5 A GND GND n_18 l=0.18u w=0.47u
Mn2 n6 inv_A GND GND n_18 l=0.18u w=0.47u
Mn3 n7 B n5 GND n_18 l=0.18u w=0.47u
Mn4 n7 inv_B n6 GND n_18 l=0.18u w=0.47u
Mn5 n8 inv_B n5 GND n_18 l=0.18u w=0.47u
Mn6 n8 B n6 GND n_18 l=0.18u w=0.47u
Mn7 S inv_C n7 GND n_18 l=0.18u w=0.47u
Mn8 S C n8 GND n_18 l=0.18u w=0.47u
.ends

```

Since I can only stick to the diagram, there is no much I can do(nothing left for me to design). I only use  $w=0.47u$  instead of  $w=0.25u$  due to the DRC in layout(physical) design.

## Bonus

## Graph

## Code



New

```

**Your code**
.subckt INV in inv_out VDD GND
Mp1 inv_out in VDD VDD p_18 l=0.18u w=0.47u
Mn1 inv_out in GND GND n_18 l=0.18u w=0.47u
.ends

**Your design**
.subckt hw2_bonus A B C S VDD GND
**Your code**
Xinv1 A inv_A VDD GND INV
Xinv2 B inv_B VDD GND INV
Xinv3 C inv_C VDD GND INV
Mn1 n1 inv_B A GND n_18 l=0.18u w=0.47u
Mp1 n1 B A VDD p_18 l=0.18u w=0.47u
Mn2 n1 B inv_A GND n_18 l=0.18u w=0.47u
Mp2 n1 inv_B inv_A VDD p_18 l=0.18u w=0.47u *A ^ B
Xinv4 n1 inv_n1 VDD GND INV
Mn3 S inv_n1 C GND n_18 l=0.18u w=0.47u
Mp3 S n1 C VDD p_18 l=0.18u w=0.47u
Mn4 S n1 inv_C GND n_18 l=0.18u w=0.47u
Mp4 S inv_n1 inv_C VDD p_18 l=0.18u w=0.47u *A ^ B ^ C
.ends

```


I have tried using n-mos only, but the voltage drop ( $V_d = \max(V_s, V_g - V_{Th})$ ), so I choose to add p-mos as trasmission gate(which can also be considered as pass transisstor method).




New

# Pre-sim waveform

## HW2

 


## Bonus

 

# Screenshot of my layout

## HW2

 

My area:  $(0.79 - (-10.78)) * (5.32 - (-1.84)) = 11.57 * 7.16 = 82.8412(\mu m^2)$

## Bonus


Drawing layout is driving me crazy, I choose not to prolong my suffering :).

Although the layout of this bonus part will be much easier, since I can design my own logic and thus save a lot of transistors (in my design, only 16, and it can be less or share some diffusion or poly).



# Screenshot of DRC summary report

## HW2

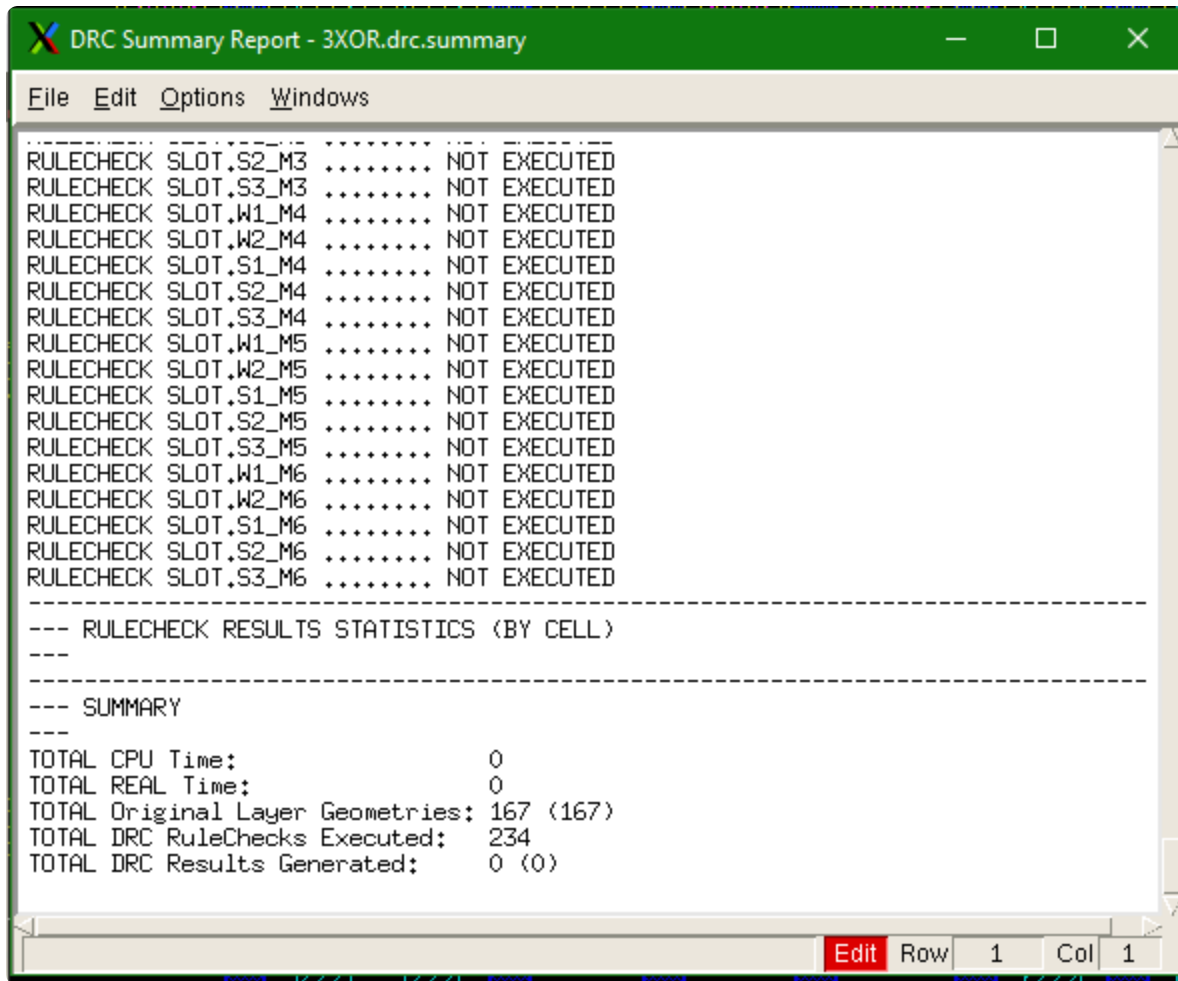

```
DRC Summary Report - 3XOR.drc.summary
File Edit Options Windows
-----
RULECHECK SLOT.S2_M3 ..... NOT EXECUTED
RULECHECK SLOT.S3_M3 ..... NOT EXECUTED
RULECHECK SLOT.W1_M4 ..... NOT EXECUTED
RULECHECK SLOT.W2_M4 ..... NOT EXECUTED
RULECHECK SLOT.S1_M4 ..... NOT EXECUTED
RULECHECK SLOT.S2_M4 ..... NOT EXECUTED
RULECHECK SLOT.S3_M4 ..... NOT EXECUTED
RULECHECK SLOT.W1_M5 ..... NOT EXECUTED
RULECHECK SLOT.W2_M5 ..... NOT EXECUTED
RULECHECK SLOT.S1_M5 ..... NOT EXECUTED
RULECHECK SLOT.S2_M5 ..... NOT EXECUTED
RULECHECK SLOT.S3_M5 ..... NOT EXECUTED
RULECHECK SLOT.W1_M6 ..... NOT EXECUTED
RULECHECK SLOT.W2_M6 ..... NOT EXECUTED
RULECHECK SLOT.S1_M6 ..... NOT EXECUTED
RULECHECK SLOT.S2_M6 ..... NOT EXECUTED
RULECHECK SLOT.S3_M6 ..... NOT EXECUTED
-----
--- RULECHECK RESULTS STATISTICS (BY CELL)
---
-----
--- SUMMARY
---
TOTAL CPU Time:                0
TOTAL REAL Time:               0
TOTAL Original Layer Geometries: 167 (167)
TOTAL DRC RuleChecks Executed:  234
TOTAL DRC Results Generated:    0 (0)
-----
Edit Row 1 Col 1
```

## Bonus

As mentioned above.



# Screenshot of LVS report includes the message of passing LVS

## HW2

Cell hw2\_XOR Summary (Clean)

CELL COMPARISON RESULTS ( TOP LEVEL )

#  
#  
# #  
# #  
#

#####  
#  
# CORRECT #  
#  
#  
#####

-

\*

\*

-

|

\\_/\_/

LAYOUT CELL NAME:hw2\_XOR

SOURCE CELL NAME:hw2\_XOR

-----

INITIAL NUMBERS OF OBJECTS

-----

LayoutSourceComponent Type

-----

Ports:66

Nets:1717

Instances:1111MN (4 pins)  
1111MP (4 pins)

-----

Total Inst:2222

NUMBERS OF OBJECTS AFTER TRANSFORMATION

-----

LayoutSourceComponent Type

-----

Ports:66

Nets:1717

Instances:88MN (4 pins)  
88MP (4 pins)  
33\_invv (4 pins)

-----

Total Inst:1919

\*\*\*\*\*

INFORMATION AND WARNINGS

\*\*\*\*\*

Matched LayoutMatched SourceUnmatched LayoutUnmatched SourceComponent Type

-----

Ports:6600

Nets:171700

Instances:8800MN(N\_18)  
8800MP(P\_18)  
3300\_invv

-----

Total Inst:191900



New




## Bonus

As mentioned above.

## Post-sim waveform

### HW2

 

## Bonus

As mentioned above.



New

# Screenshot of the post-simulation result

## HW2

```
*****
**110060012_hw2_xor**

***** transient analysis tnom= 25.000 temp= 30.000 *****
power= 18.2489u from= 0. to= 50.0000n
delay1_xor= -2.0337n targ= 17.9813n trig= 20.0150n
delay2_xor= -2.0086n targ= 3.0064n trig= 5.0150n

***** job concluded
*****
**110060012_hw2_xor**
```

## Bonus

As mentioned above.

**Write down your delay and the difference in delay between rising and falling delay in the 3-input XOR gate.**

## HW2

### Pre-sim

```
*****
**110060012_hw2_xor**

***** transient analysis tnom= 25.000 temp= 30.000 *****
power= 11.3806u from= 0. to= 50.0000n
delay1_xor= -2.1901n targ= 17.8249n trig= 20.0150n
delay2_xor= -2.1801n targ= 2.8349n trig= 5.0150n

| | | ***** job concluded
*****
**110060012_hw2_xor**
```

$$Delay1_{XOR} = -2190.1ps$$

$$Delay2_{XOR} = -2180.1ps$$

$$|Delay1_{XOR} - Delay2_{XOR}| = 10ps$$

## Post-sim

```
*****
**110060012_hw2_xor**

***** transient analysis tnom= 25.000 temp= 30.000 *****
power= 18.2489u from= 0. to= 50.0000n
delay1_xor= -2.0337n targ= 17.9813n trig= 20.0150n
delay2_xor= -2.0086n targ= 3.0064n trig= 5.0150n

***** job concluded
*****
**110060012_hw2_xor**
```

$$Delay1_{XOR} = -2033.7ps$$

$$Delay2_{XOR} = -2008.6ps$$

$$|Delay1_{XOR} - Delay2_{XOR}| = 25.1ps$$

## Bonus

### Pre-sim

```
*****
**110060012_hw2_bonus**

***** transient analysis tnom= 25.000 temp= 30.000 *****
power= 7.6692u from= 0. to= 50.0000n
delay1_xor= -2.3665n targ= 17.6485n trig= 20.0150n
delay2_xor= -2.3675n targ= 2.6475n trig= 5.0150n

| | | ***** job concluded
*****
**110060012_hw2_bonus**
```

$$Delay1_{XOR} = -2366.5ps$$

$$Delay2_{XOR} = -2367.5ps$$

$$|Delay1_{XOR} - Delay2_{XOR}| = 1ps$$

## Post-sim

As mentioned above.

# The hardness of this assignment and how you overcome it

---

First of all, the issues caused by incompatible environment have made my layout-drawing journey unnecessary long and thorny. I tried Ubuntu(my major OS) first, the remote terminal kept saying that I have no sudoer permission(BadName, so I have to install something remotely). Then I tried my Mac, which worked after I installed some X11 forwarding tools, while it's extremely slow. I had no other choice but switch to windows and installed mobaXterm, not knowing there were a whole bunch of other problems were waiting for me. First of all, I think the tutorial of Virtuoso is incomplete, and the online sources is very limited. For example, if I use the whole .sp file in the LVS process instead of .cir file with the circuit only, there will be some undebuggable errors. It took me almost a day to find out the reason. Second of all, a lot of important thing haven't been demonstrated in the video, and these are not easy to figure out by merely reading the pdf provided.

## Any suggestions about this programming assignment

---

I think the tutorial video could be more thorough, so that a lot of troubles and discussions on eeclass can be saved. And most of the problems on eeclass get really prompt responses, I can sense the efforts TA put into that. Thanks for the hard work!



New